

FULL SUBTRACTOR

EXP.NO: 24

AIM:

To design and implement the full subtractor using Logisim simulator.

PROCEDURE:

- 1) Pick and place the necessary gates.
- 2) Insert 3 inputs into the canvas.
- 3) Connect the inputs to the XOR gate, AND gate and OR gate.
- 4) Insert 2 outputs into the canvas.
- 5) Make the connections using the connecting wires.
- 6) Verify the truth table.


TRUTH TABLE:

Inputs			Outputs	
A	B	Borrow _{in}	Diff	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$\text{Diff} = (A \oplus B) \oplus \text{'Borrowin'}$$

$$\text{Borrow} = A'.B + (A \oplus B)$$

OUTPUT

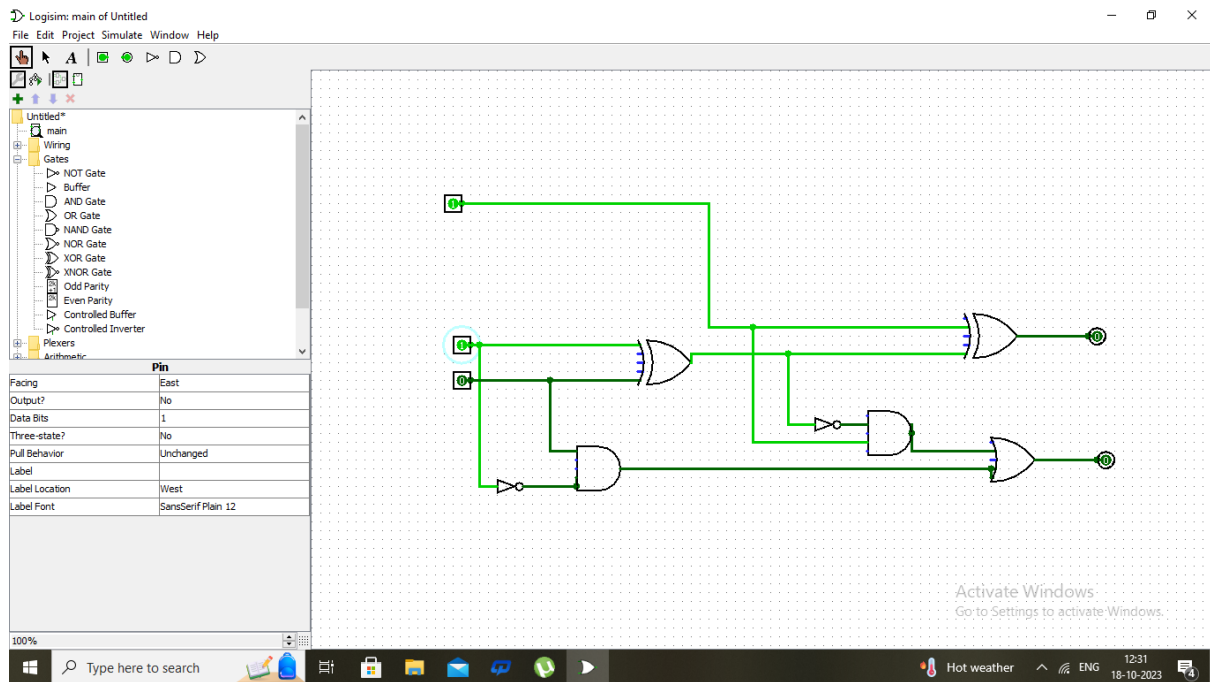

RESULT:

Thus

full subtractor has been designed and implemented successfully using logisim simulator.